

35.) R, L sorosan  $\varphi_1 = \frac{\pi}{3}$   $U_{eff,1} = U_{eff,2} = U_{eff}$   $f_2 = 2f_1$   $\frac{P_2}{P_1} = ?$

$$\omega = 2\pi f$$

$$P = I_{eff}^2 R$$


valós  
áttag  
teljesítmény

$$\tan \varphi = \frac{L\omega - \frac{1}{\omega C}}{R}$$

$$I_{eff} = \frac{U_{eff}}{Z}$$

$$Z = \sqrt{R^2 + (L\omega - \frac{1}{\omega C})^2}$$

csak R és L

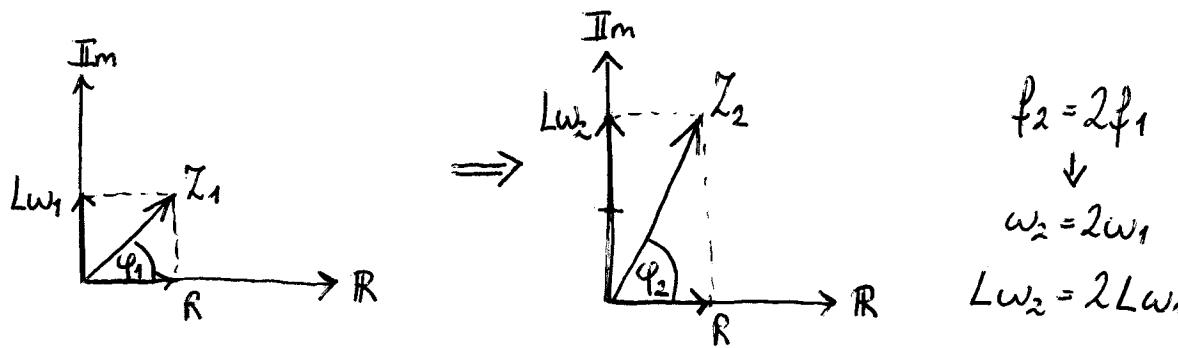

$$\tan \varphi_1 = \frac{L\omega_1}{R} \rightarrow L\omega_1 = \tan \varphi_1 \cdot R \quad (1)$$

$$\frac{P_2}{P_1} = \frac{I_{eff,2}^2 R}{I_{eff,1}^2 R} = \frac{\frac{U_{eff}^2}{Z_2^2}}{\frac{U_{eff}^2}{Z_1^2}} = \frac{Z_1^2}{Z_2^2} = \frac{R^2 + (L\omega_1)^2}{R^2 + (L\omega_2)^2} = \frac{R^2 + (L\omega_1)^2}{R^2 + (2L\omega_1)^2} = \dots$$