

21.)

$$R=100\Omega \quad L=0,2\text{H} \quad C=20\mu\text{F} \quad f=50\text{Hz} \quad U_{\text{eff}}=230\text{V}$$

a.) $I_0=?$ $I_{\text{eff}}=?$ $P=?$

b.) $\phi_r=?$ c.) $f=f_r$ $I_{0r}=?$ $I_{\text{eff}r}=?$ $P_r=?$

$$Z = \sqrt{R^2 + \left(L\omega - \frac{1}{\omega C}\right)^2} \quad I_{\text{eff}} = \frac{U_{\text{eff}}}{Z} \quad I_0 = I_{\text{eff}} \cdot \sqrt{2}$$

$$f_r = \frac{1}{2\pi\sqrt{LC}}$$

$$P = I_{\text{eff}}^2 R$$

a.) $Z = \sqrt{R^2 + \left(L\omega - \frac{1}{\omega C}\right)^2} = \dots \quad I_{\text{eff}} = \frac{U_{\text{eff}}}{Z} = \dots \quad I_0 = I_{\text{eff}} \cdot \sqrt{2} = \dots$

$$P = I_{\text{eff}}^2 R = \dots$$

b.) $f_r = \frac{1}{2\pi\sqrt{LC}} = \dots$

c.) resonancia $\rightarrow Z=R$

$$I_{\text{eff}r} = \frac{U_{\text{eff}}}{R} = \dots \quad I_0 = I_{\text{eff}} \cdot \sqrt{2} = \dots$$

$$P_R = I_{\text{eff}r}^2 \cdot R = \dots$$