

37.) $U_{\text{eff}} = 108 \text{ V}$ L, C és r (tekercs ellenállása) f változik

$f_1 = 25 \text{ Hz}$ $I_{\text{eff}1} = 8 \text{ A}$ $\frac{P_r}{P_0} = ?$

$$f_r = \frac{1}{2\pi\sqrt{LC}} \quad \omega = 2\pi f$$

$f_2 = 55 \text{ Hz}$ $I_{\text{eff}2} = 24 \text{ A}$ maximális!

$$Z = \frac{U_{\text{eff}}}{I_{\text{eff}}}$$

$L, C = ?$ $r = ?$

$$Z = \sqrt{R^2 + (L\omega - \frac{1}{\omega C})^2}$$

Mivel $I_{\text{eff}2}$ maximális \rightarrow rezonancia

$$f_2 = f_r = \frac{1}{2\pi\sqrt{LC}} \rightarrow (1) \quad 4\pi^2 f_2^2 L = \frac{1}{C}$$

$Z_2 = Z_r = r$ (rezonancia!) $Z_2 = r = \frac{U_{\text{eff}}}{I_{\text{eff}2}} = \dots$

$$Z_1 = \frac{U_{\text{eff}}}{I_{\text{eff}1}} = \sqrt{r^2 + (L\omega - \frac{1}{\omega C})^2}$$

\Downarrow

$$L$$

\Downarrow

$$C = \frac{1}{4\pi^2 f_2^2 L} = \dots$$

$$\frac{P_r}{P_0} = \frac{I_{\text{eff}1}^2 \cdot r}{I_{\text{eff}1} \cdot U_{\text{eff}}} = \frac{I_{\text{eff}1} \cdot r}{U_{\text{eff}}} = \frac{I_{\text{eff}1} \cdot r}{I_{\text{eff}1} \cdot Z_1} = \frac{r}{Z_1} = \dots$$